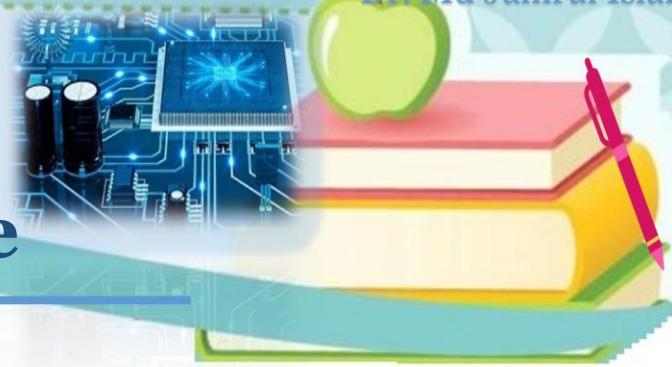


EE 2240: Electrical and Electronic Circuit Simulation Laboratory

Credit- 1.5

Course Teachers: Dr. Md. Jahirul Islam
&
Dr. Md. Tawabur Rahman

- **References:**
 - 1st & 2nd Years' Electrical Circuit and Electronics Books
 - <https://saadat.us/pspiceintro201.htm>
 - <https://home.olemiss.edu/>
 - Other online sources




Course Information Outline

- **TOPIC 1:** Introduction to Electronic Circuit Simulation and Software Packages


- **TOPIC 2: Circuit Simulation with PSPICE**

- **TOPIC 3:** Circuit Simulation with PROTEUS

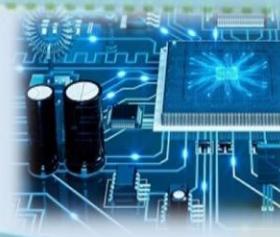- **TOPIC 4:** Introduction to MATLAB and Circuit Simulation with MATLAB




Practice-3.1: DC Power Supply

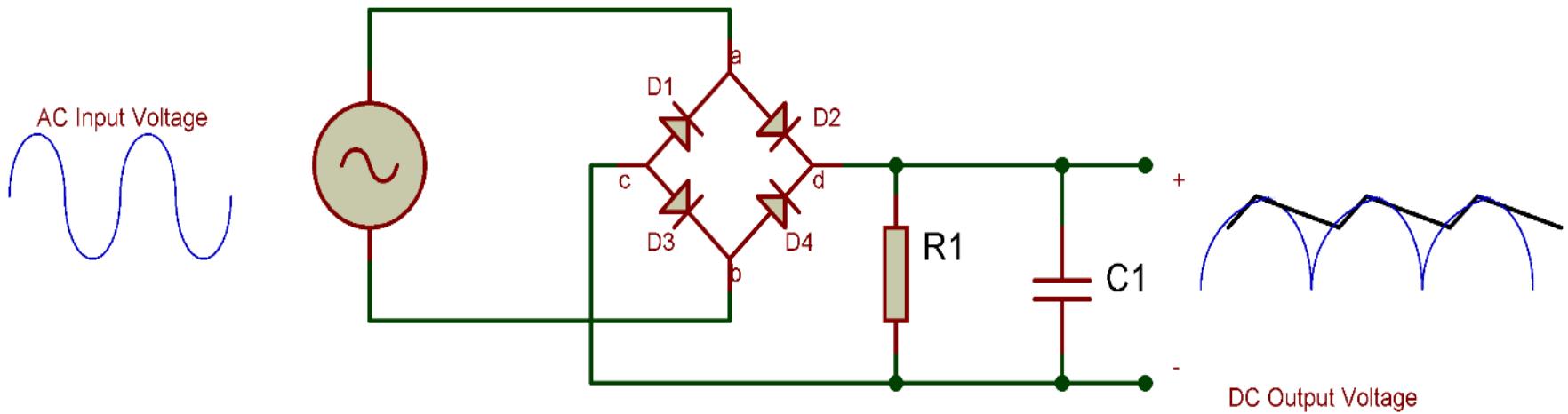





Practice-3.2: User Defined Source

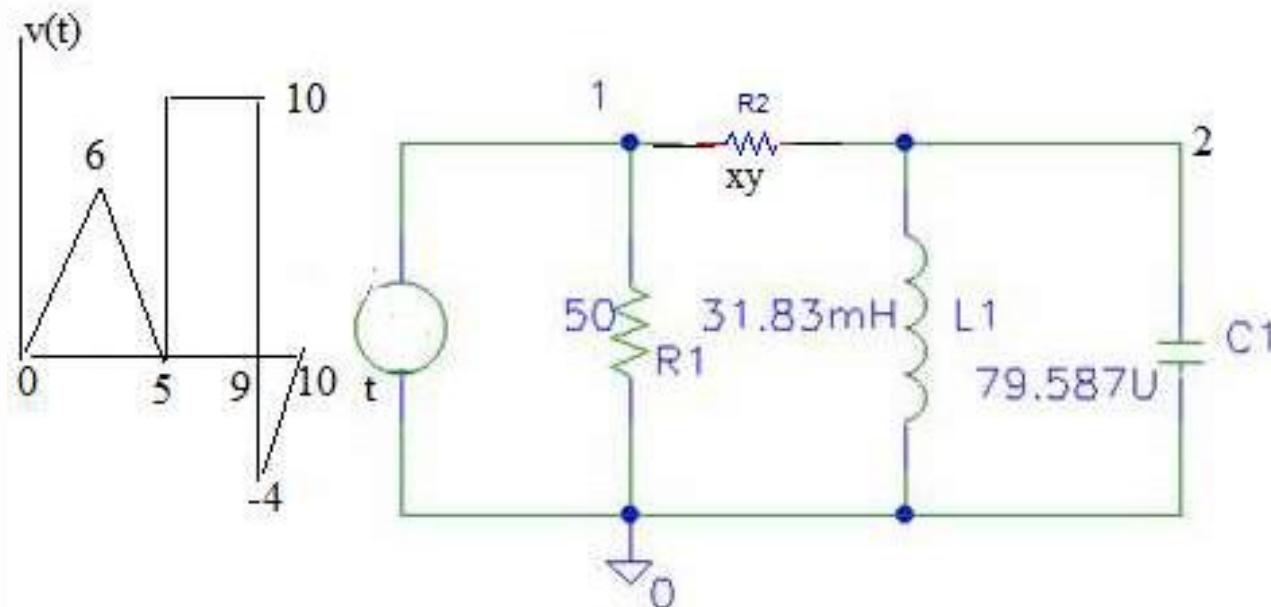- For the parallel RLC circuit shown, plot the voltages at points 1 and 2 when the user-defined input as given is applied.



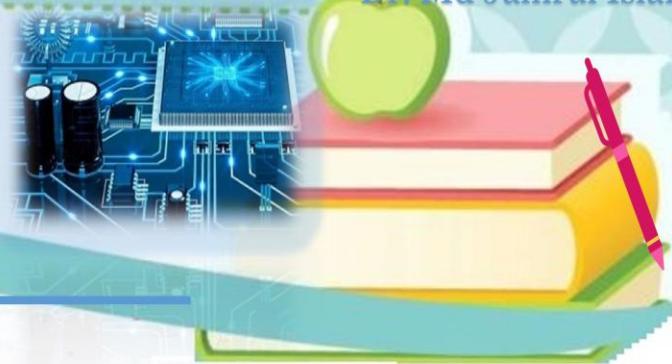

Practice-3.3: CE VDB Amplifier Circuit

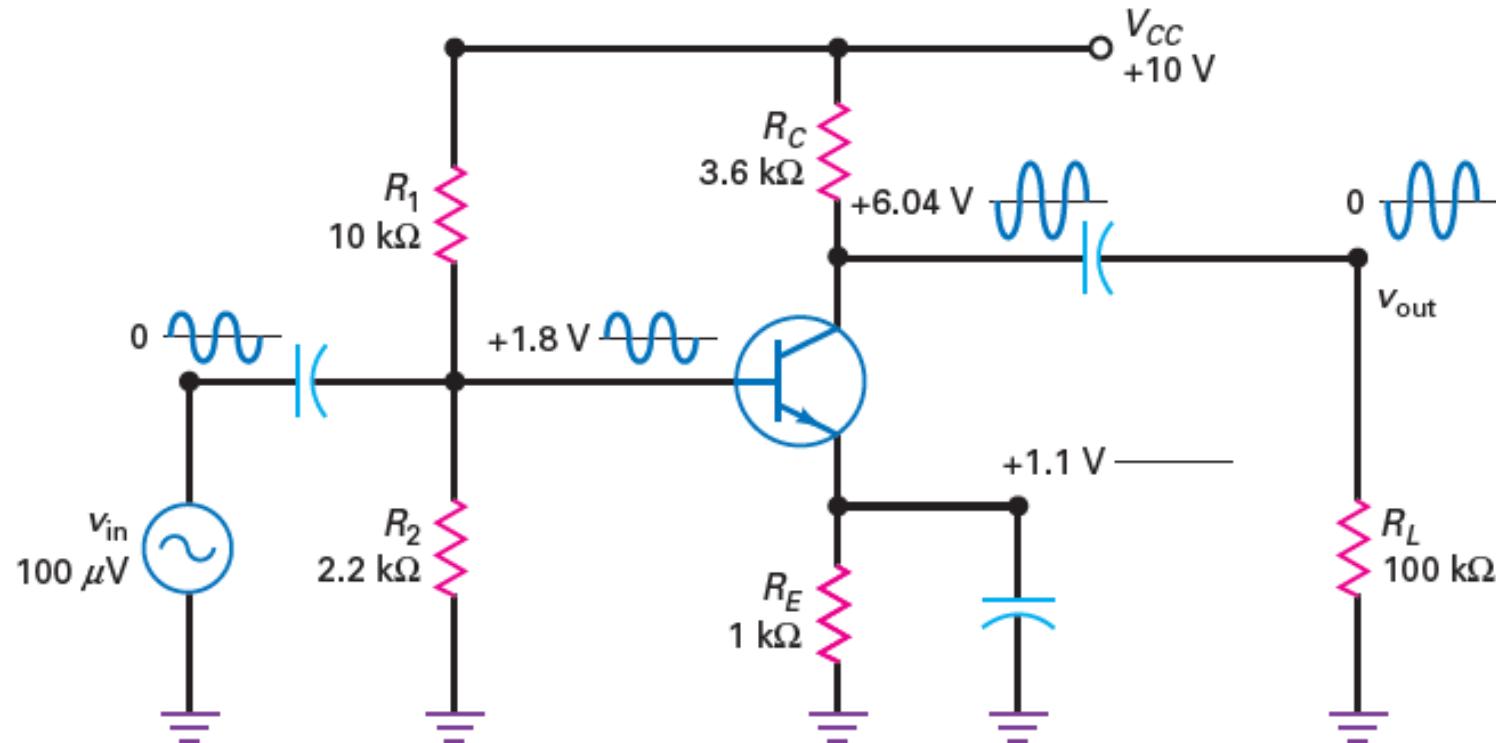



Practice-3.4: OP-amp Amplifier Circuit

