
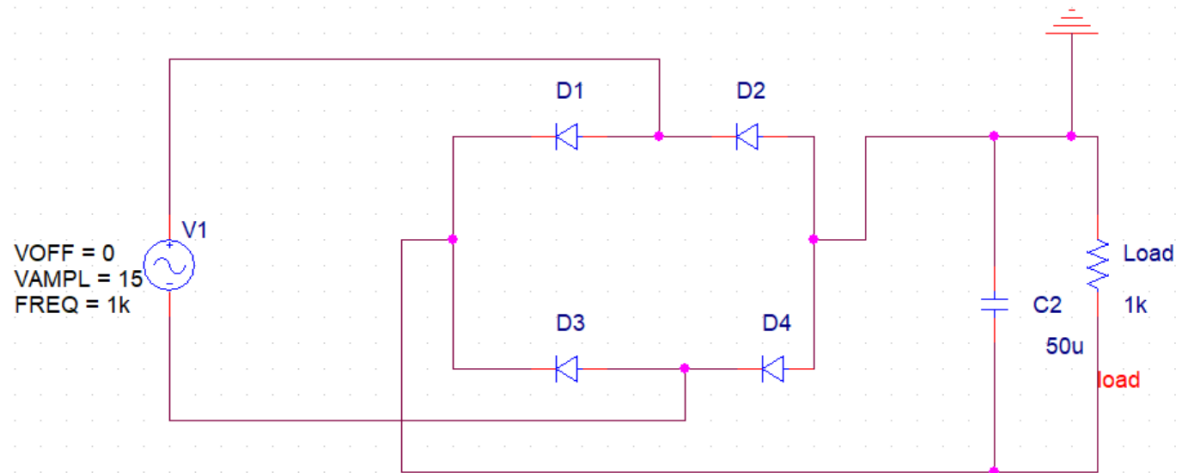


Practice Problems:

Practice1: Full Wave Bridge rectifier(For DC voltage supply)

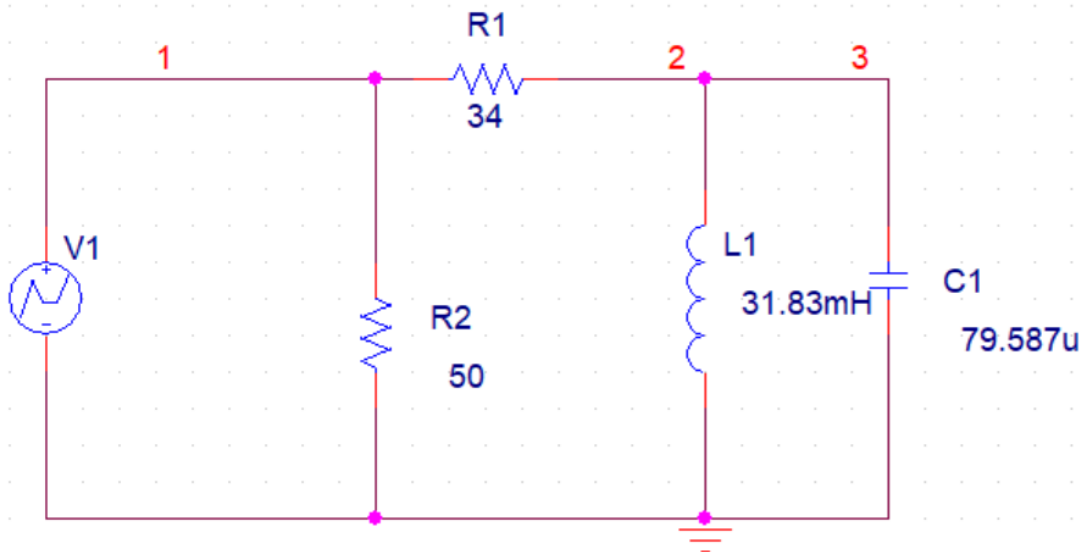


Practice2: User defined input in a RLC circuit



C:\Users\pc\OneDrive\Desktop\test3.txt

Practice2: Inverting Operational Amplifier using LM741

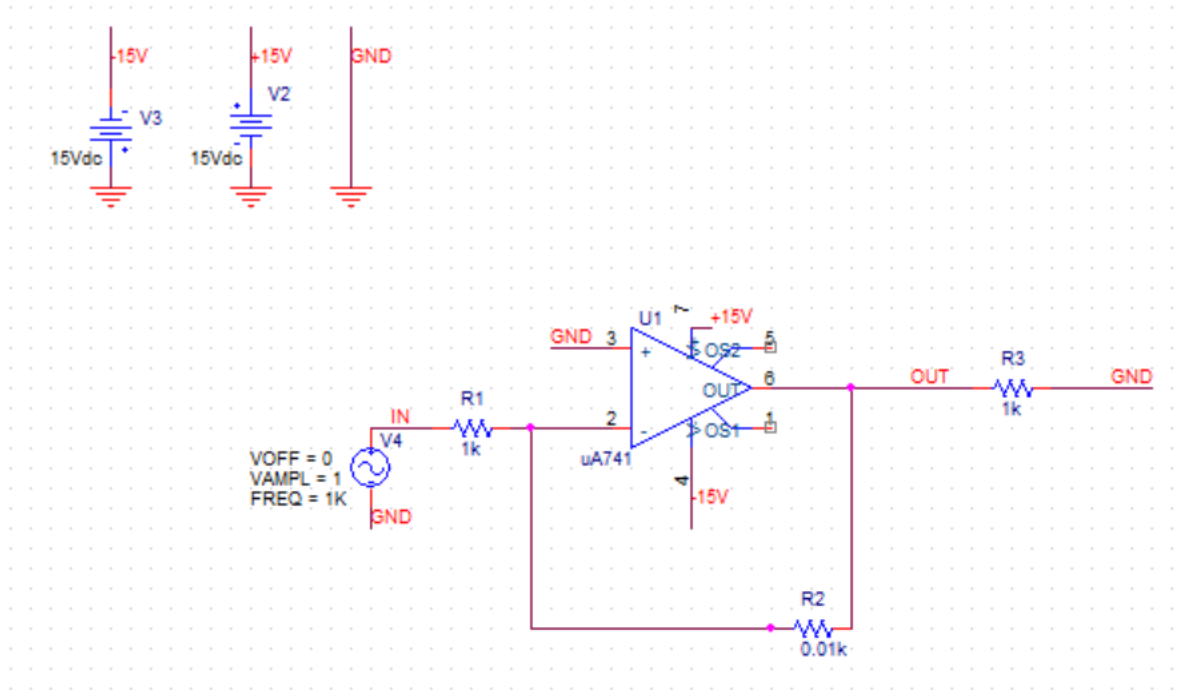

Practice4: Common-Emitter Voltage Divider Amplifier circuit

